 


Digital project

VHDL – Intro +

useful things

FSM (finite state machine), if time.



Outline

- Why VHDL?
- HDL vs “regular programming language”
- The basics
- An example
 - Contains the basics of the basics
 - If you understand it you can pass the course!
- Common pitfalls!
- State machines if time (otherwise next time)

HDL – Code

VHDL:

VHSIC Hardware Description Language

Very High Speed Integrated Circuit

(Verilog)

Used for:

- Description
- Simulation
- Synthesis

Mor info : Part-1 VHDL Basic

Why VHDL?

- HDL is the method for designing digital systems today. (VHDL or VERILOG)
- VHDL is originally designed for simulation.
- **Simulation and synthesis to hardware are two different things!**

VHDL - just looks like a program!

Common program

- Compiled
- Runs on a processor
- **Strictly in sequence**
- (Possibly multiple processors)

VHDL

- Simulated (~ effective)
- Translated into hardware
- **Strictly parallel**
- Simulation and hardware differ in several ways.

VHDL “lingo”

- Two things always go together in VHDL
 - Not that “module” is not a VHDL term though!
- **Entity** declaration
 - Defines the external interface to the module
- **Architecture** body
 - The stuff that describes what a module does internally
 - Different types of architectures
 - Multiple architectures can be bound to one entity

Define Module

Define a module and specify I/O Ports to add to your source file.
For each port specified:
MSB and LSB values will be ignored unless its Bus column is checked.
Ports with blank names will not be written.

Module Definition

Entity name:

Architecture name:

I/O Port Definitions

+ - ↑ ↓

Port Name	Direction	Bus	MSB	LSB	
	in	<input type="checkbox"/>	0	0	

?

OK Cancel

In

Out

InOut – Avoid, if you do not have a bidirectional signal

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MyMux is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          C : in STD_LOGIC;
          Ctrl : in STD_LOGIC;
          Ut : out STD_LOGIC);
end MyMux;

architecture Behavioral of MyMux is

begin
    -- write your
    A = B -- Syntax error is highlighted
    -- code here
end Behavioral;
```


Example: Simple AND gate

```
-- AND gate
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY and2 IS
    PORT (ain:IN STD_LOGIC;
          bin:IN STD_LOGIC;
          cout:OUT STD_LOGIC);
END and2;


ARCHITECTURE arch_and2 OF and2 IS
BEGIN
    cout<=ain AND bin;
END arch_and2;
```

Libraries with
built-in functions


Entity

Architecture

 VHDL - Looks like programming.
but the differences are significant


 
```
-- AND gate  
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
  
ENTITY and2 IS  
    PORT (ain:IN STD_LOGIC;  
          bin:IN STD LOGIC;  
          cout:OUT STD_LOGIC) ;  
END and2;
```



```
ARCHITECTURE arch_and2 OF and2 IS  
BEGIN  
    cout<=ain AND bin;  
END arch_and2;
```

More info : Part-1 VHDL Basic

VHDL basics cont.

Example

Entity

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
  
ENTITY and_or IS  
    PORT (  
        a:IN STD_LOGIC;  
        b:IN STD_LOGIC;  
        c:IN STD_LOGIC;  
        y_conc:OUT STD_LOGIC;  
        y_seq:OUT STD_LOGIC);  
END and_or;
```

If we look at the code from another perspective we can also see two types of code inside the architecture

- *Concurrent code*

Parallel code, things happen at the same time

- Sequential code

The code is interpreted in a sequence, line by line

Such code has to be written in a **process**

The whole process is concurrent with other code

We focus on sequential code!

Example concurrent vs sequential code

Architecture

Internal signals —

```
ARCHITECTURE arch_and_or OF and_or
IS
  SIGNAL x_conc:STD_LOGIC;
  SIGNAL x_seq:STD_LOGIC;
```

BEGIN

Concurrent code —

```
    x_conc <= a AND b;
    y_conc <= x_conc OR c;
```

Process name —

```
    seq: PROCESS (a, b, c)
    BEGIN
```

Sequential code —

```
        x_seq <= a AND b;
        y_seq <= x_seq OR c;
    END PROCESS seq;
END arch_and_or;
```

Sensitivity list

The signals that trigger
(activate) the process

The sensitivity list
ONLY has to do
with simulation!

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY and_or IS
  PORT (
    a:STD_LOGIC;
    b:STD_LOGIC;
    c:IN STD_LOGIC;
    y_conc:OUT STD_LOGIC;
    y_seq:OUT
    STD_LOGIC);
END and_or;
```



Basic VHDL structures

CASE statement

The CASE statement has similarities to the WITH statement.

The structure is

```
[Case label:]  
CASE selectorSignal IS  
    WHEN value1 =>  
        sequential code;  
    WHEN value1 =>  
        sequential code;  
    [WHEN value2 =>  
        sequential code;]  
    [WHEN others =>  
        sequential code;]  
END CASE [Case label];
```

The CASE label is optional but it enhances the readability of the code

If the WHEN cases don't cover all of the possible values for selectorSignal we must include the OTHERS clause

All cases have the same priority

VHDL Ex

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following lines to use the declarations that are
-- provided for instantiating Xilinx primitive components.
--library UNISIM;
--use UNISIM.VComponents.all;
--*      Led0
--*      ----
--* Led5 |Led6| Led1
--*      ----
--* Led4 |Led3| Led2
--*      ----
entity Bcd2Led is
  Port ( Bcd : in std_logic_vector(3 downto 0);
        Led : out std_logic_vector(6 downto 0));
end Bcd2Led;
```

architecture Behavioral of Bcd2Led is

begin

p1:process(Bcd)

begin

case Bcd is

when "0000"=>

Led<="1111110"; -- 0

when "0001"=> Led<="0110000"; -- 1

when "0010"=> Led<="1101101"; -- 2

when others => null; -- the rest

end case;

end process;

end Behavioral;

```

Port ( Ctrl : in std_logic_vector(1 downto 0);
      A : in std_logic_vector(3 downto 0);
      B : in std_logic_vector(3 downto 0);
      C : in std_logic_vector(3 downto 0);
      Ut : out std_logic_vector(3 downto 0));
end MyMux;

```

architecture Behavioral of MyMux is

Begin

p1:process(Ctrl,A,B,C)

begin

case Ctrl is

when "00"=>Ut<=A;

when "01"=> Ut<=B;

when "10"=> Ut<=C;


when others => Ut<="1010";-- the rest

end case;

end process p1;

end Behavioral;

mymux

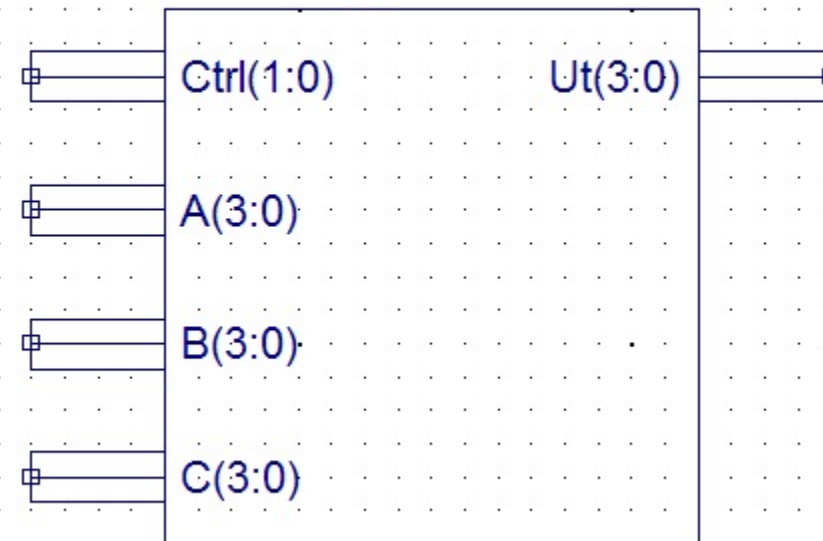

*when "00"=>
Ut<=A;*

VHDL basics cont.

Basic VHDL structures

IF statement cont.

Examples

BAD

```
IF (a='0') THEN  
    y <= '1';  
END IF;
```

Basic IF structure. Avoid since we don't give any value to y when a='1'.

This means that we need a memory element, a flip-flop, to remember the value when the IF statement is false

GOOD

```
IF (a='0') THEN  
    y <= '1';  
ELSE  
    y <= '0';  
END IF;
```

IF structure with complete assignment.
Use this instead.


No memory element needed

VHDL – Synthesis

Clocked processes must be sensitive to one flank.

Use the features **rising_edge(clk)**

 - Make plausibility analysis on number of gates and number of latches. Study the gate schematic after synthesis.
- "Think Hardware"
 - Think of hardware when writing the VHDL code.
(unfortunately requires training and experience)



NOTE! Synthesis!
The simulator
can do without

VHDL basics cont.

Basic VHDL structures

Free in
Xilinx

Synchronous code with asynchronous reset

Basic structure

```
async_reset: PROCESS (clk, reset)
BEGIN
    IF (reset = '1') THEN
        asynchronous_reset_code;
    ELSIF (rising_edge(clk)) THEN
        synchronous_main_code;
    END IF;
END PROCESS async_reset;
```

Both signals must be able to trigger the process

No other signals should be included in the sensitivity list

Level triggered reset


Positively edge triggered clk signal

rising_edge(clk)

Think in hardware when writing VHDL. Ex

- A traffic counter should be designed.
- It shall calculate the number of wheels traveling north and the number traveling south.
- When a car travels over the sensor, a pulse of B_n and B_s is generated.
- Should only one pulse occur, B_n or B_s , the system should return after a timeout and wait for a new pulse.

Traffic counter

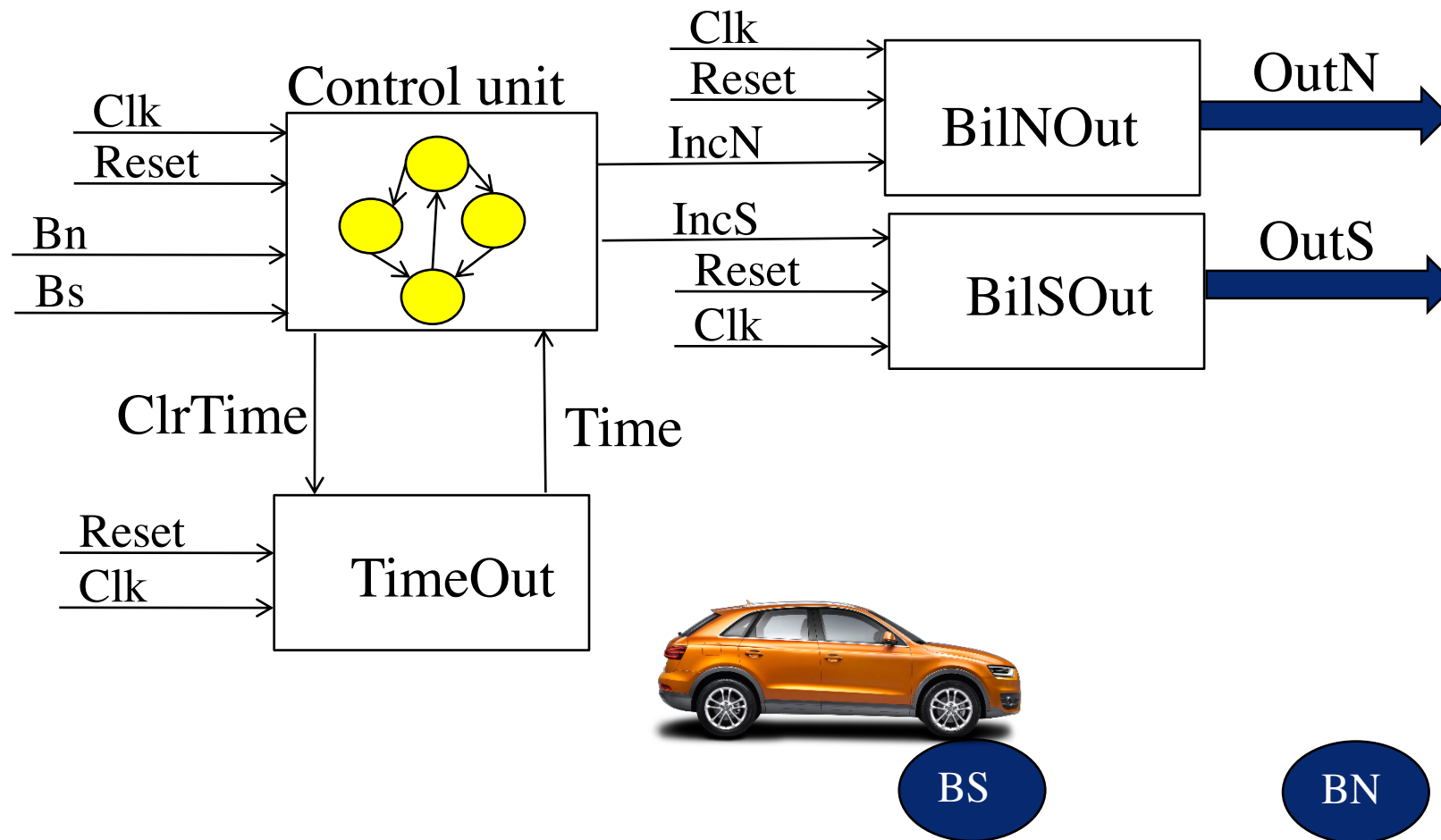

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use ieee.std_logic_unsigned.all;

```

ENTITY TrafikM **IS**

```

generic (nc : NATURAL := 8;
          nt : NATURAL := 3);

```

```

PORT(Reset:IN STD_LOGIC;
      Clk:IN STD_LOGIC;
      Bn:IN STD_LOGIC;
      Bs:IN STD_LOGIC;


```

```

      Outn : out std_logic_vector (nc-1 downto 0);
      Outs : out std_logic_vector (nc-1 downto 0));

```

END TrafikM;

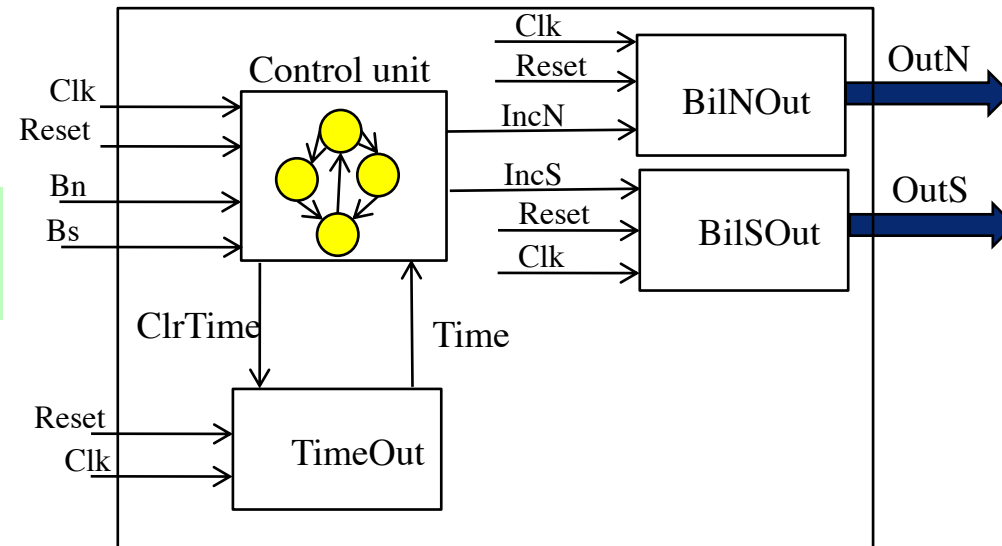

ARCHITECTURE arch_TrafikM **OF** TrafikM **IS**
SIGNAL Time : std_logic_vector (nt-1 downto 0);
BEGIN

TimeOut : **process** (Clk, Reset) **is**

variable cnt : std_logic_vector (nt-1 **downto** 0);

begin

if Reset = '1' **then**

cnt := (**others** => '0');

elsif rising_edge(Clk) **then**

if ClrTime='1' **then**

cnt := (**others** => '0');

else

cnt := cnt+1;



end if; -- ClrTime

end if;

Time <= cnt;

end process TimeOut;

1 process

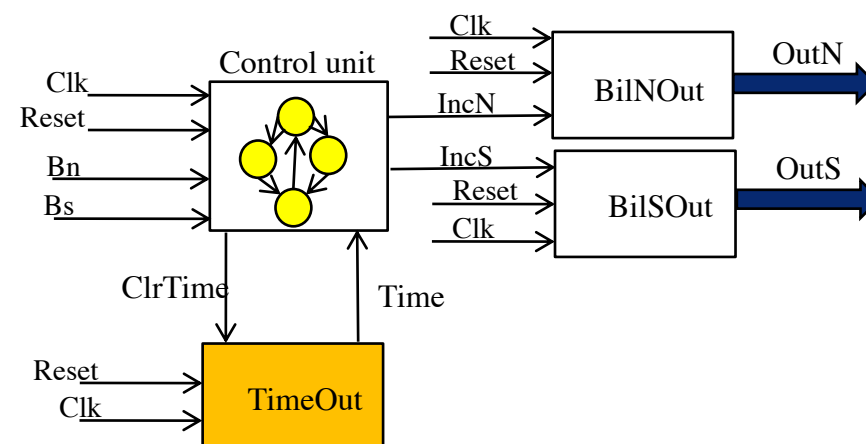 

CMem : **process** (Clk, Reset) **is**
begin

if Reset = '1' **then**

 Time <= (others => '0');

elsif rising_edge(Clk) **then**

 Time <= Next_TC;

end if;

end process CMem;

TimeOut : **process** (ClrTime, Time) **is**
begin

if ClrTime='1' **then**

 Next_TC <= (others => '0');



else

 Next_TC <= Time + 1;

end if; -- ClrTime

end process TimeOut;

2 processes

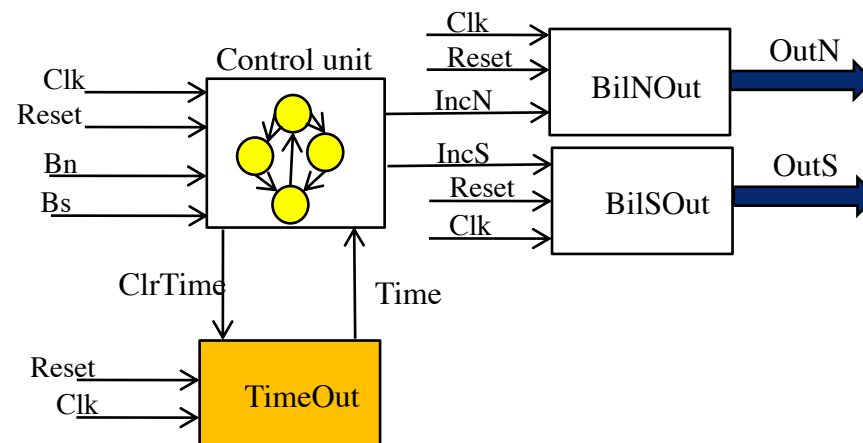 

ARCHITECTURE arch_TrafikM2 **OF** TrafikM2 **IS**

SIGNAL Norr_Cnt, Next_Norr

: std_logic_vector (nc-1 downto 0);

...

BEGIN

CMem : process (Clk, Reset) is

begin

if Reset = '1' then

Time <= (others => '0');

Norr_Cnt <= (others => '0');

elsif rising_edge(Clk) then

Time <= Next_TC;

Norr_Cnt <= Next_Norr;

end if;

end process CMem;

BilNOut : **process** (IncN, Norr_Cnt) **is**
begin

if IncN='1' **then**

Next_Norr <= Norr_Cnt+1;


else


Next_Norr <= Norr_Cnt;

end if; -- CnUppS

end process BilNOut;

OutN <= Norr_Cnt; -- **OBS!!**

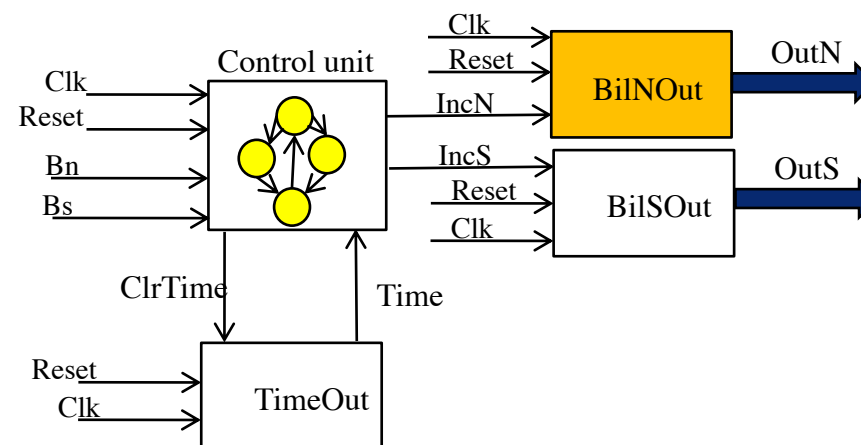

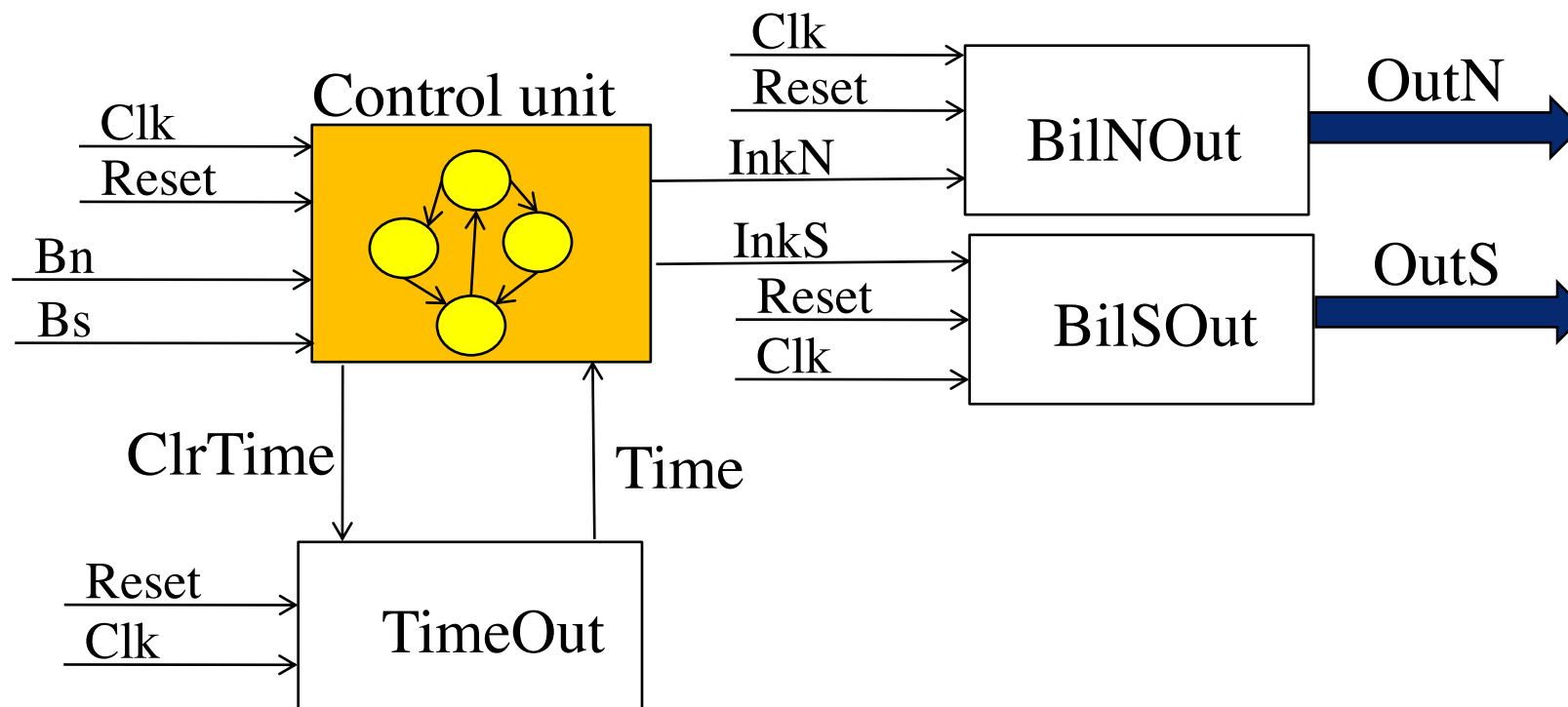

ARCHITECTURE arch_TrafikM2 OF TrafikM2 IS

TYPE state_type **is** (Start, BilS, BilN, VerS, VerN);


SIGNAL State, Next_State : state_type;


SIGNAL Time, Next_TC : std_logic_vector (nt-1 downto 0);

SIGNAL Norr_Cnt, Next_Norr, Sod_Cnt, Next_Sod : std_logic_vector (nc-1 downto 0);

SIGNAL ClrTime, IncS, IncN : STD_LOGIC;

BEGIN

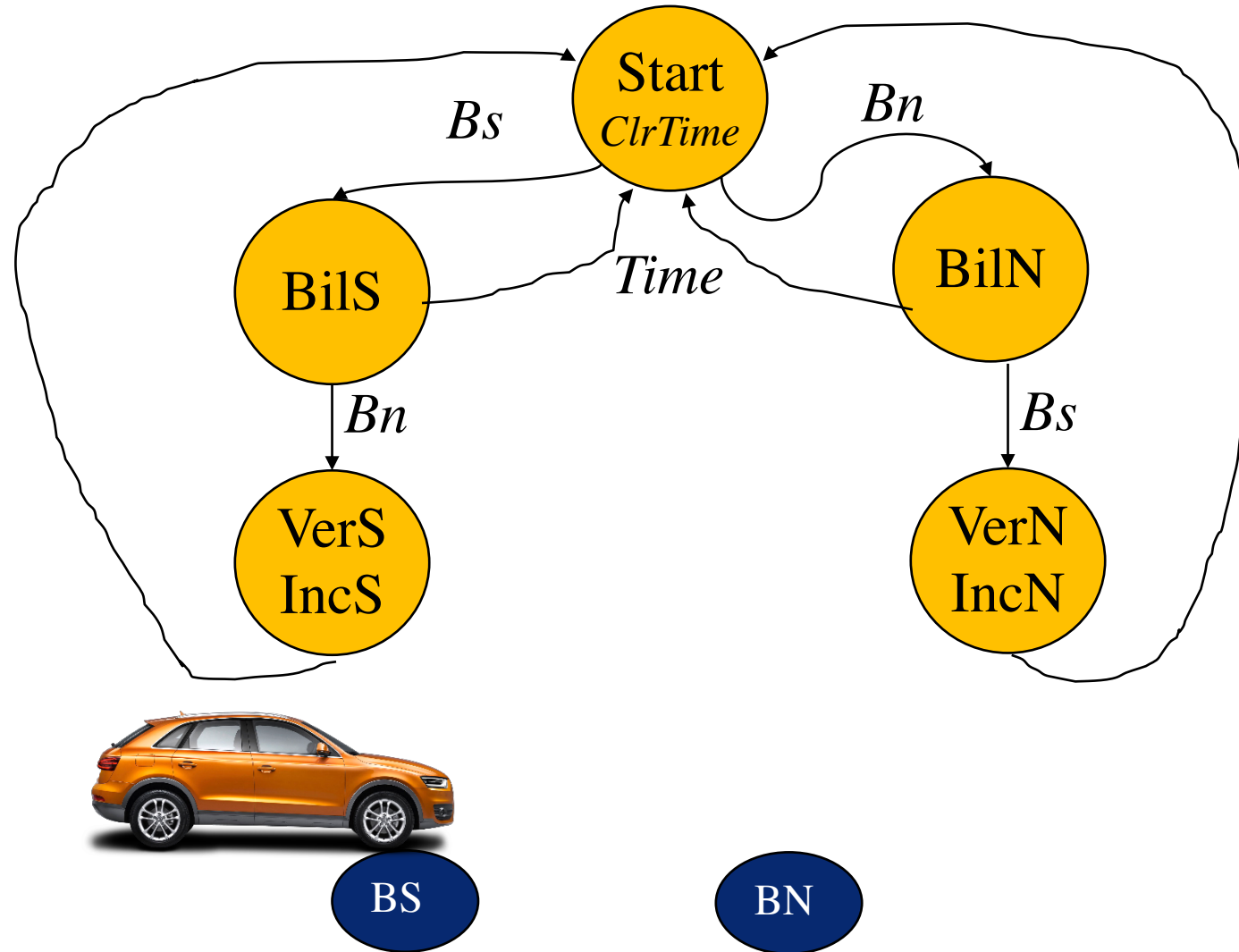

 

```

Kombinatorisk: process(state, FC)
begin
  A<='0'; B<='0' -- DEFAULT
  case state is
    when Start=>
      A<='1';
      if FC ='1' then next_state<= Fc1;
      else next_state<=Start;
      end if;
    when Fc1=>
      B<='1';
      next_state<= PB;
    when PB=>
      B<='1';
      next_state<= Start;
  end case;
end process Kombinatorisk;
  
```


```

p1: process(Clk)
begin
  if Clk'event and Clk='1' then
    if Reset='1' then
      state<=Start;
    else
      state<=next_state;
    end if;
  end if;
end process p1;
  
```

```

CMem : process (Clk, Reset) is
begin
  if Reset = '1' then
    Time <= (others => '0');
    Norr_Cnt <= (others => '0');
    Sod_Cnt <= (others => '0');
    State <= Start;
  elsif rising_edge(Clk) then
    Time <= Next_TC;
    Norr_Cnt <= Next_Norr;
    Sod_Cnt <= Next_Sod;
    State <= Next_State;
  end if;
end process CMem;

```

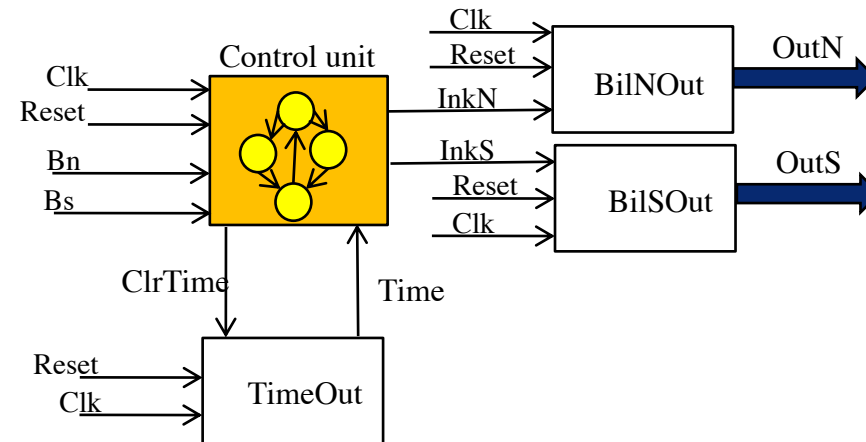

```
FSM : process (State, Bn, Bs, Time) is
begin
```

```
  ClrTime <='0'; IncS <='0'; IncN <='0';
```

```
  case State is
```

```
    when Start =>
```

```
      ClrTime <='1';
```

```
      if Bs='1' then
```

```
        Next_State <= BilS;
```

```
      elsif BN='1' then
```

```
        Next_State <= BilN;
```

```
      else
```

```
        Next_State <= Start;
```

```
      end if;
```

```
    when BilS =>
```

```
      if Bn='1' then
```

```
        Next_State <= VerS;
```

```
      elsif Time(nt-1)='1' then
```

```
        Next_State <= Start;
```

```
      else Next_State <= BilS; end if;
```

```
    when BilN =>
```

```
      if Bs='1' then Next_State <= VerN;
```

```
      elsif Time(nt-1)='1' then
```

```
        Next_State <= Start;
```

```
      else Next_State <= BilN;
```

```
      end if;
```

```
    when VerS => IncS <='1';
```

```
      Next_State <= Start;
```

```
    when VerN => IncN <='1';
```


```
      Next_State <= Start;
```

```
    when others =>
```

```
      Next_State <= Start;
```

```
  end case;
```

```
end process FSM;
```

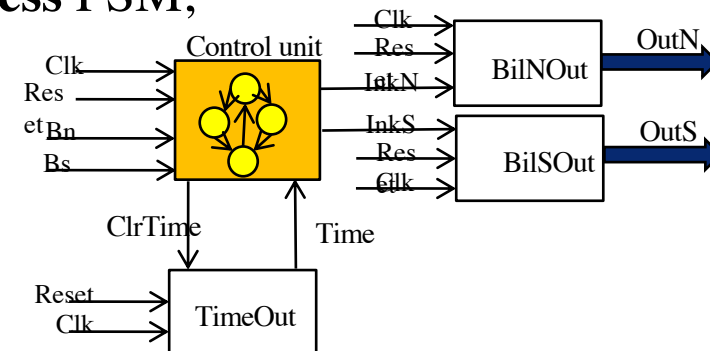

```


FSM : process (State, Bn, Bs, Time) is
begin
  ClrTime <='0'; IncS <='0'; IncN <='0';
  Next_State <= Start;
  case State is
    when Start =>
      ClrTime <='1';
      if Bs='1' then
        Next_State <= BilS;
      elsif BN='1' then
        Next_State <= BilN;
      end if;
    when BilS =>
      if Bn='1' then
        Next_State <= VerS;
      elsif Time(nt-1)='0' then
        Next_State <= BilS;
      end if;
  end case;
end process FSM;

```

```

when BilN =>
  if Bs='1' then Next_State <= VerN;
  elsif Time(nt-1)='0' then
    Next_State <= BilN;
  end if;
when VerS => IncS <='1';
when VerN => IncN <='1';
when others =>
end case;
end process FSM;

```

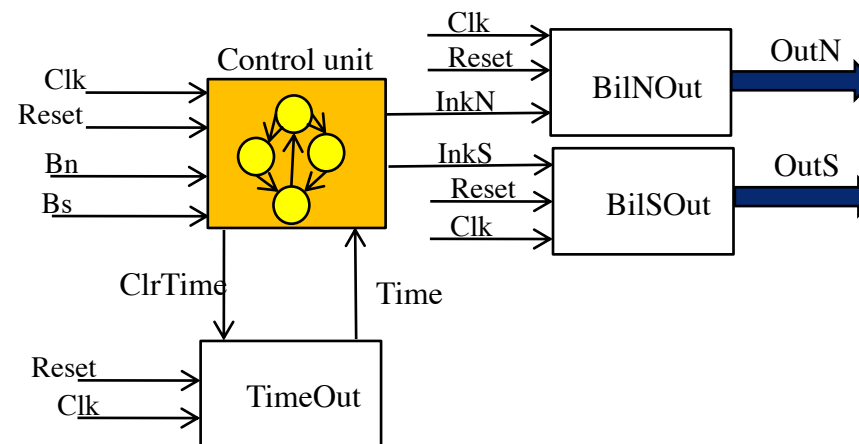

Package

- To reduce the need for declarations
- To use the same types everywhere
- To use common features

- For the more advanced
- Use records declared in package


```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
  
PACKAGE MyPac IS  
  COMPONENT full_adder IS  
    PORT (  
      a:IN STD_LOGIC;  
      b:IN STD_LOGIC;  
      cin:IN STD_LOGIC;  
      y:OUT STD_LOGIC  
      cout:OUT STD_LOGIC);  
  END COMPONENT full_adder;  
END MyPac;
```

USE work.MyPac.all;

Add:
Generics
Constants
Types
Component
Declarations

HERE!


Summary

VHDL is used for

Description / Specification / Documentation
of hardware.

- Simulation of hardware.
- Synthesis of hardware.

Entity - Architecture

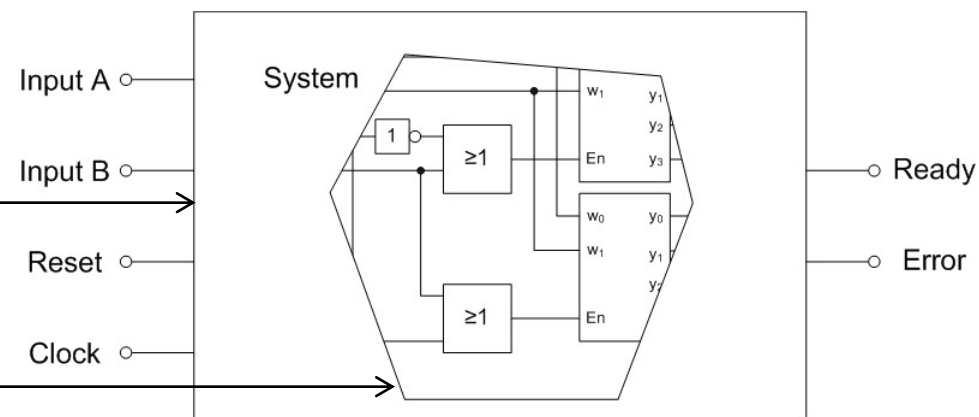

- VHDL – A "strongly typed" language
- Library :
Library IEEE;
use IEEE.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.numeric_std.all; ← Newer better
- Signal assignments \leq (*At END of PROCESS*)
- Variable assignments $:=$ (*Immediately*)
- *It is possible to use variables to simplify for oneself.*

”Implicit memory”

- The value is retained if no assignment
- D-flip-flop (Register / counter etc.)
- **IF rising_edge(Clk) THEN**
- Asynchronous Reset

```
cnt2 : process (Clk, Reset) is  
begin
```

```
    if Reset = '1' then <Reset Statements >
```

```
    elsif rising_edge(Clk) then
```

```
        <Statements>;
```

```
    end if;
```

” Synchronous Reset”

- **cnt2 : process (Clk) is**
begin
if rising_edge(Clk) then
 if Reset = '1' then <Reset Statements >
 else
 <Statements>;
 end if; -- Reset
end if; -- Clk'EVENT


To do:

- Tutoring times.
- Mo 13-15, Wh 10-12, Fr 10-12 (*week 3*)
- *Select project - as soon as possible*
(*You who have not done so yet*)
- Book time for weekly meeting

Block diagram!


State machine

Moore model


 


State machine

Mealy model

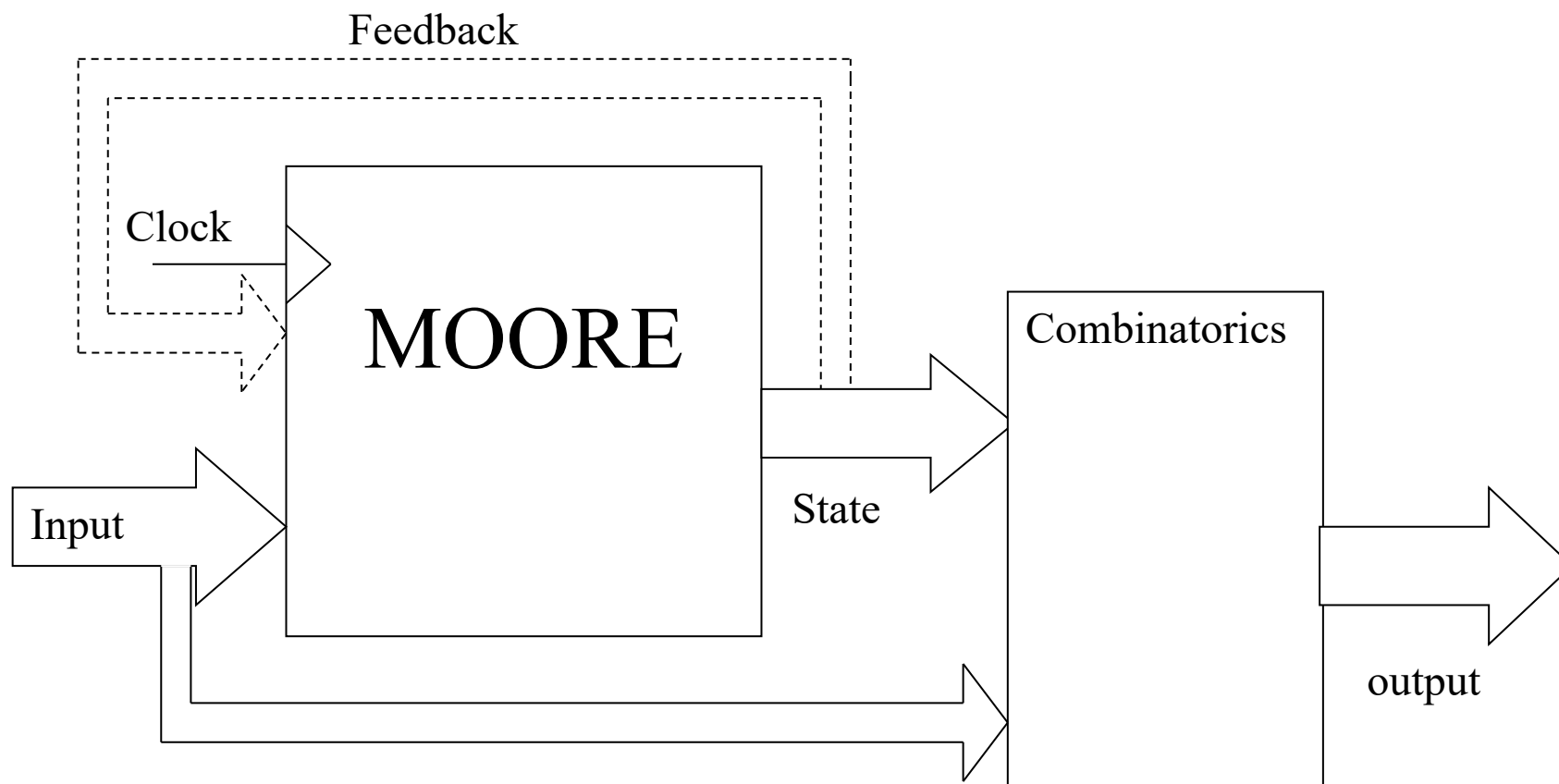


Hazard

  

State machine


2-ways to get the output

State action

 

Moore

Transaction action

 

Mealy

WHEN zero=>



O<="01"; -- Moore output

IF I='1' THEN


next_state <=one1;

O<="10"; -- Mealy output



END IF;

  

State action (Moore)

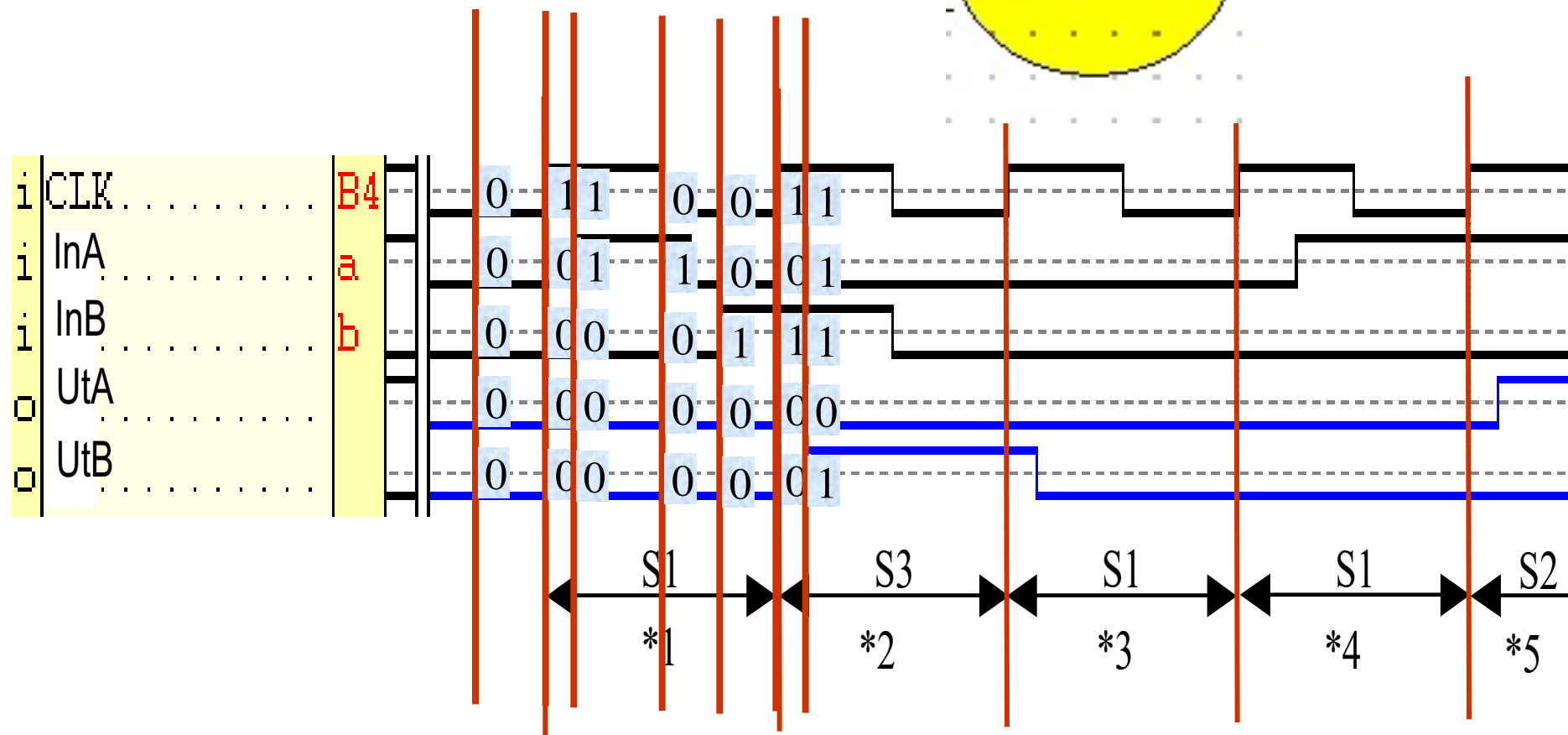

Transaction action (Mealy)

 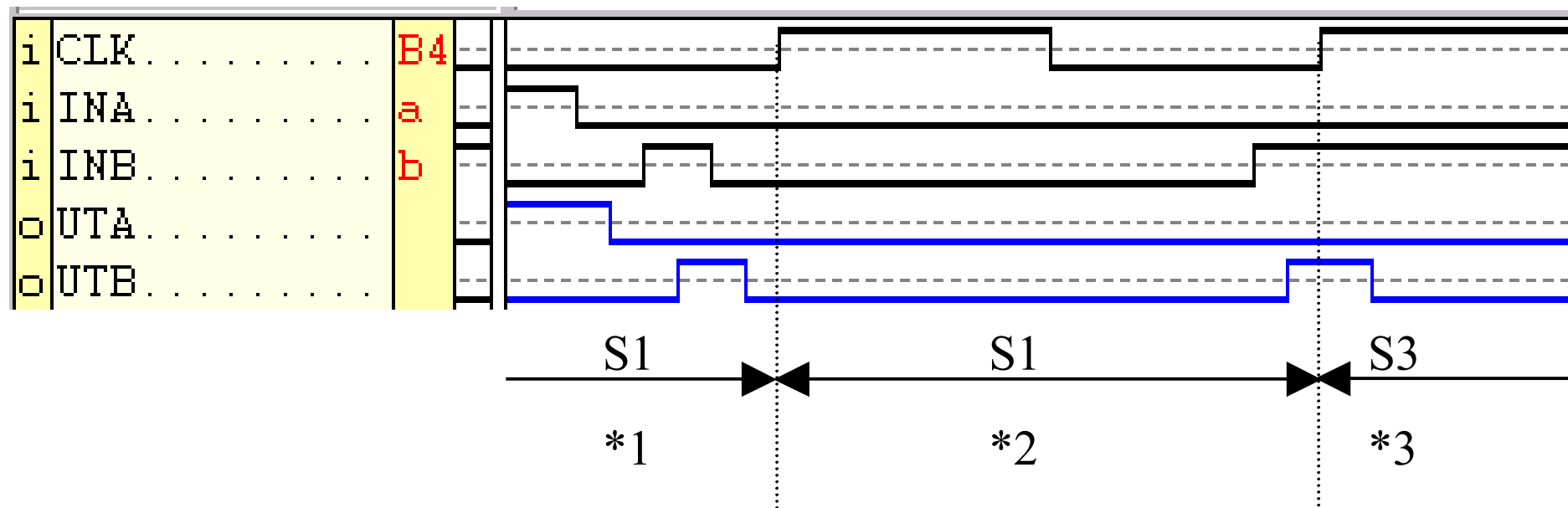


Summary state machines

```
-- Synchronous process
ASM_P: PROCESS (Clk,Reset)
BEGIN
  IF Reset = '1' THEN -- Asynkron
    reset
    state<=zero; -- Reset tillstand
  ELSIF rising_edge(CLK) THEN
    state<=next_state;
    SO<= O -- Synkron Mealy output
  END IF;
END PROCESS ASM_P;
```


```
next_s:PROCESS (state,I)
BEGIN
  next_state <=zero; -- default
  O<="00";
  CASE state IS
    WHEN zero=>
      O<="01"; -- Moore output
      IF I='1' THEN
        next_state <=one1;
        O<="10"; -- Mealy output
      END IF;
```

...

Structure

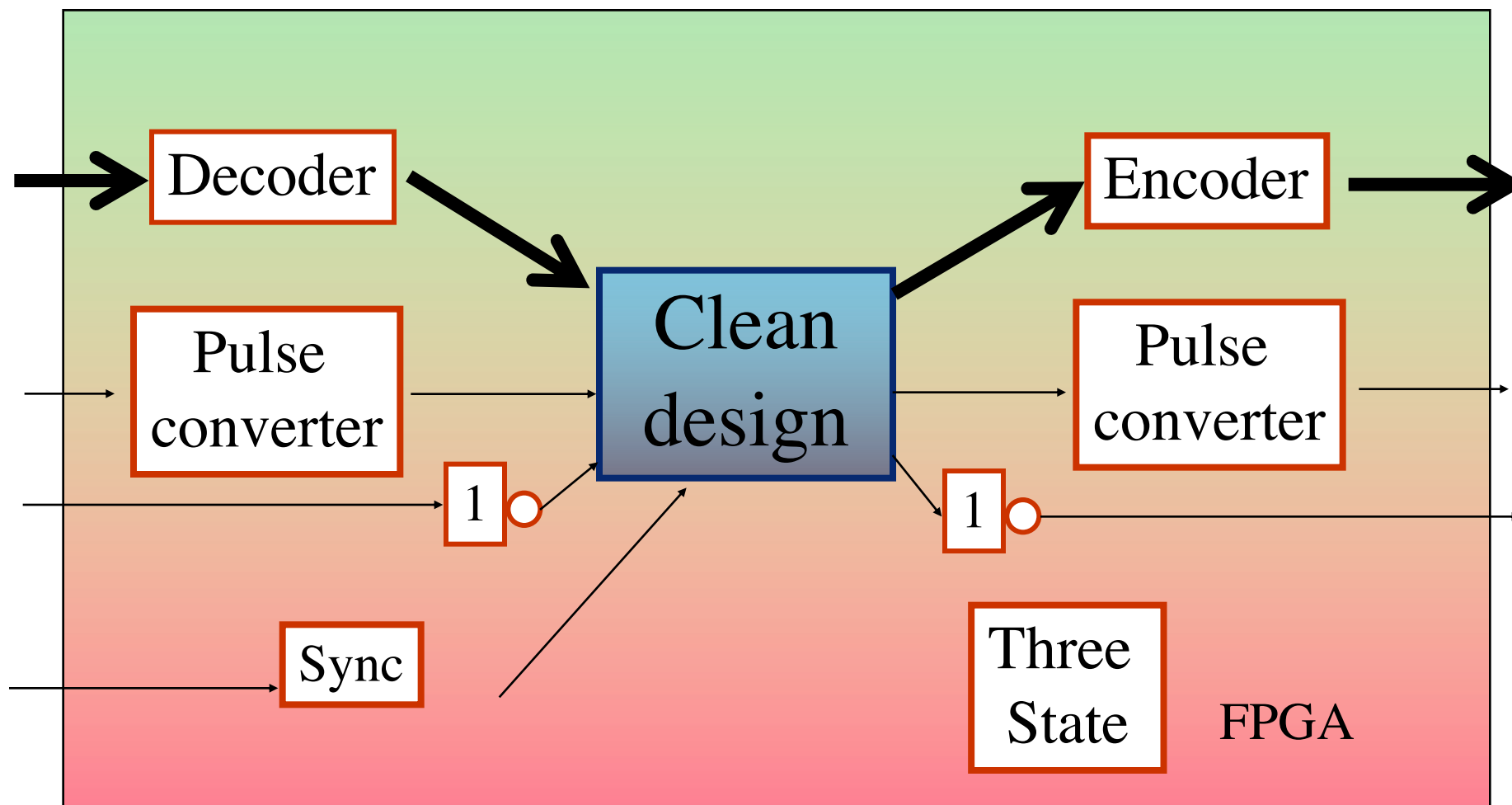

Pulse to level converter

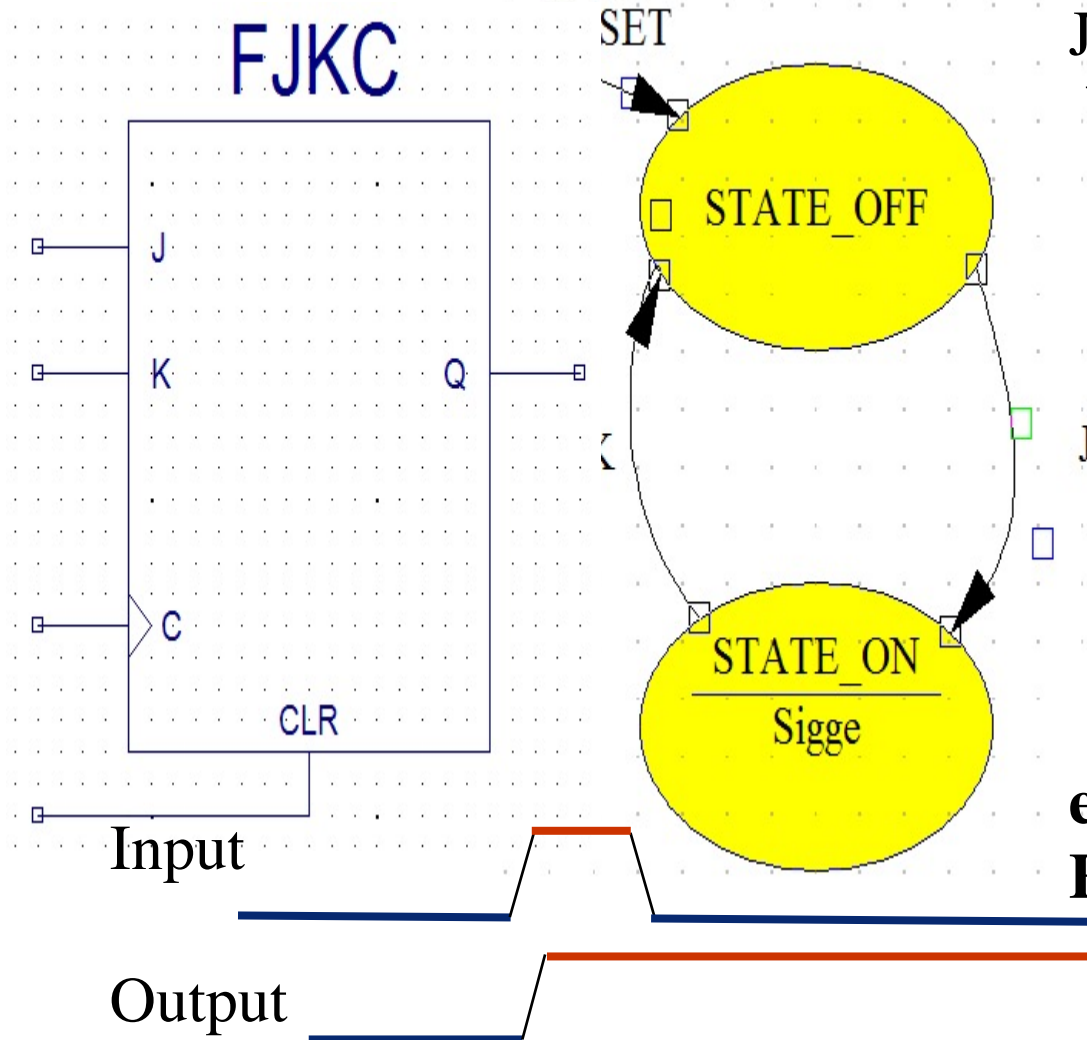

JK Vippa : process (Clk, Reset) is
begin

if Reset = '1' then Y <= '0';

elsif **rising_edge**(Clk) then

if J = '1' and K = '1' then

Q <= not Q;

elsif J = '1' then Q <= '1';

elsif K = '1' then Q <= '0';


end if; -- **JK**


end if; -- **Reset**

end process JK Vippa;

END arch_FPGA_D;

Level to pulse converter

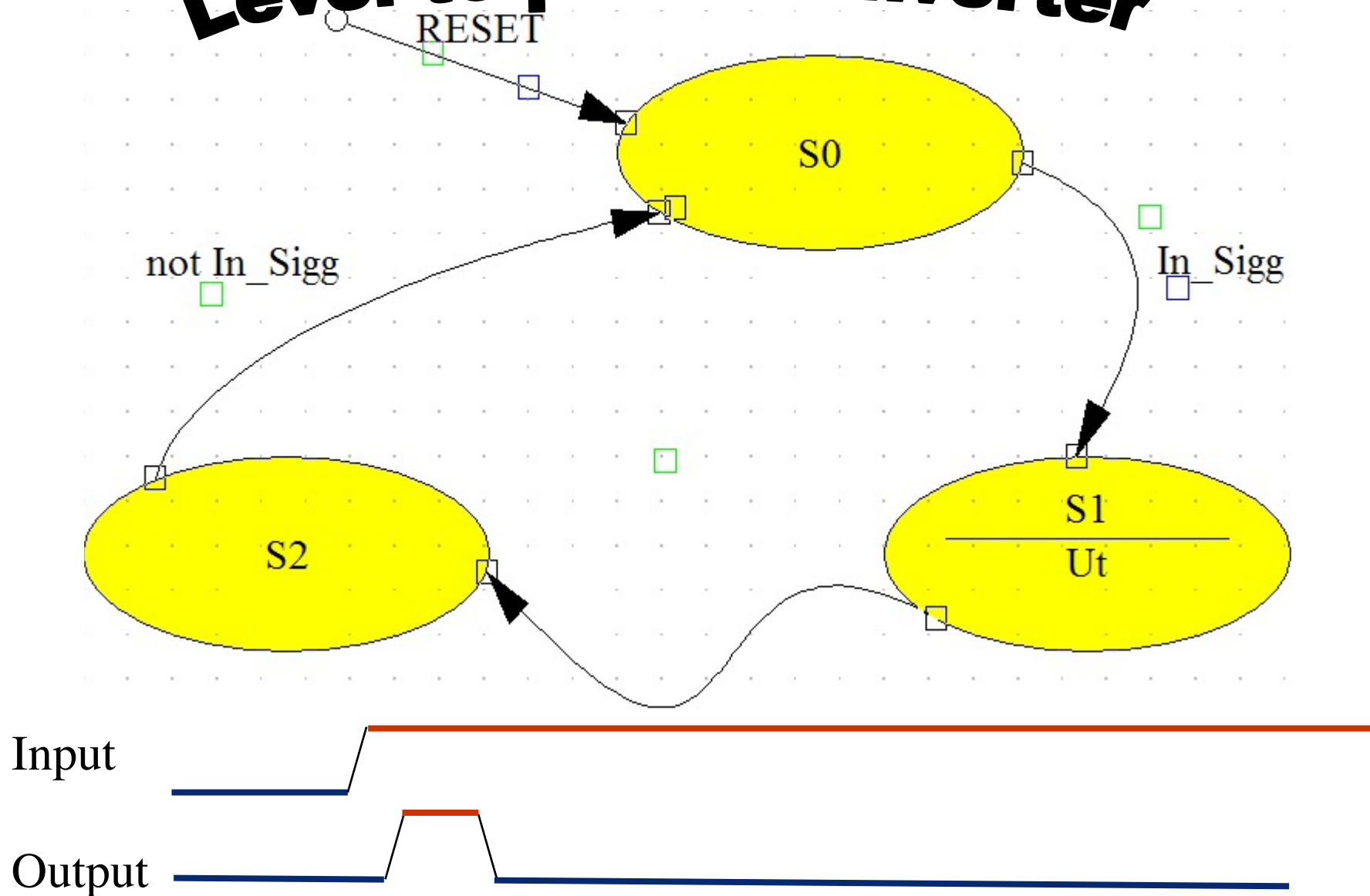

 

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

```

```

ENTITY pin IS
PORT (
  Din, En : IN STD_LOGIC;
  OutSig : INOUT STD_LOGIC);
END pin;

```

```

ARCHITECTURE Bet OF pin IS
BEGIN

```

```

  PROCESS (Din,En) IS
BEGIN

```

```

    IF En='1' THEN

```

```

      OutSig <= Din;

```

```

    ELSE

```

```

      OutSig <= 'Z';

```

```

    END IF; -- En

```

```

  END PROCESS;

```



```

END Bet;

```

Handle asynchronous inputs

  
- **Never, Never, Never** allow asynchronous inputs to be connected to more than one flip-flop
- synchronize as soon as possible and then process the signal as synchronous




```

next_s:PROCESS (state,I)
BEGIN
  next_state <=zero; -- default
CASE state IS
  WHEN zero=>
    O<="01"; -- Moore output
    IF I='0' THEN
      next_state <=one1;
      O<="10"; -- Mealy output
    END IF;



```

 

Coding

 

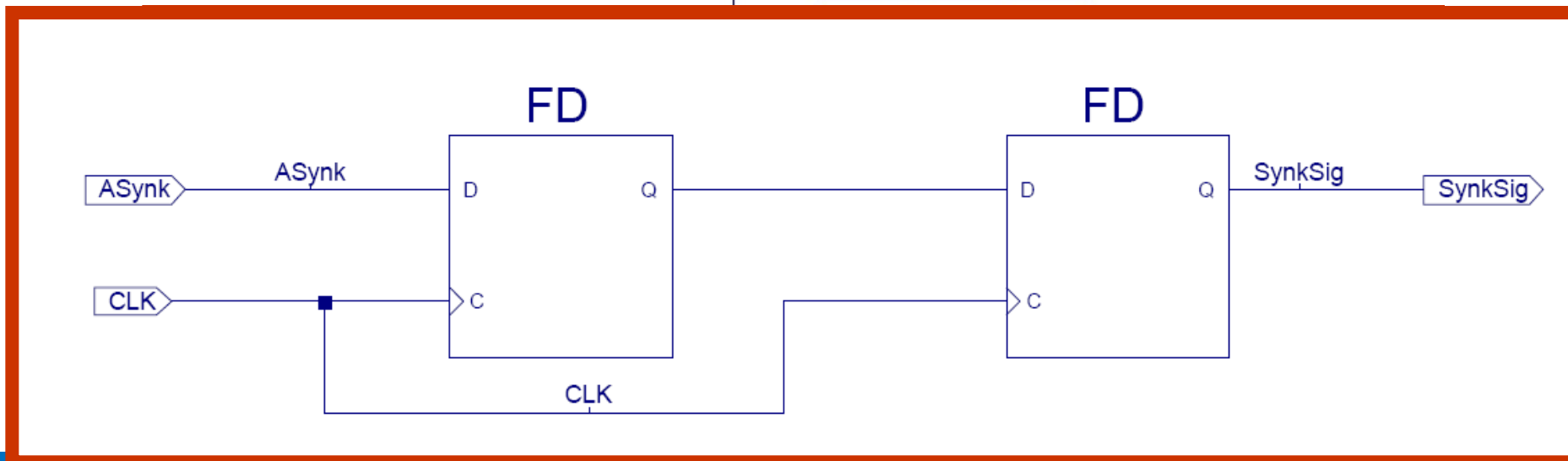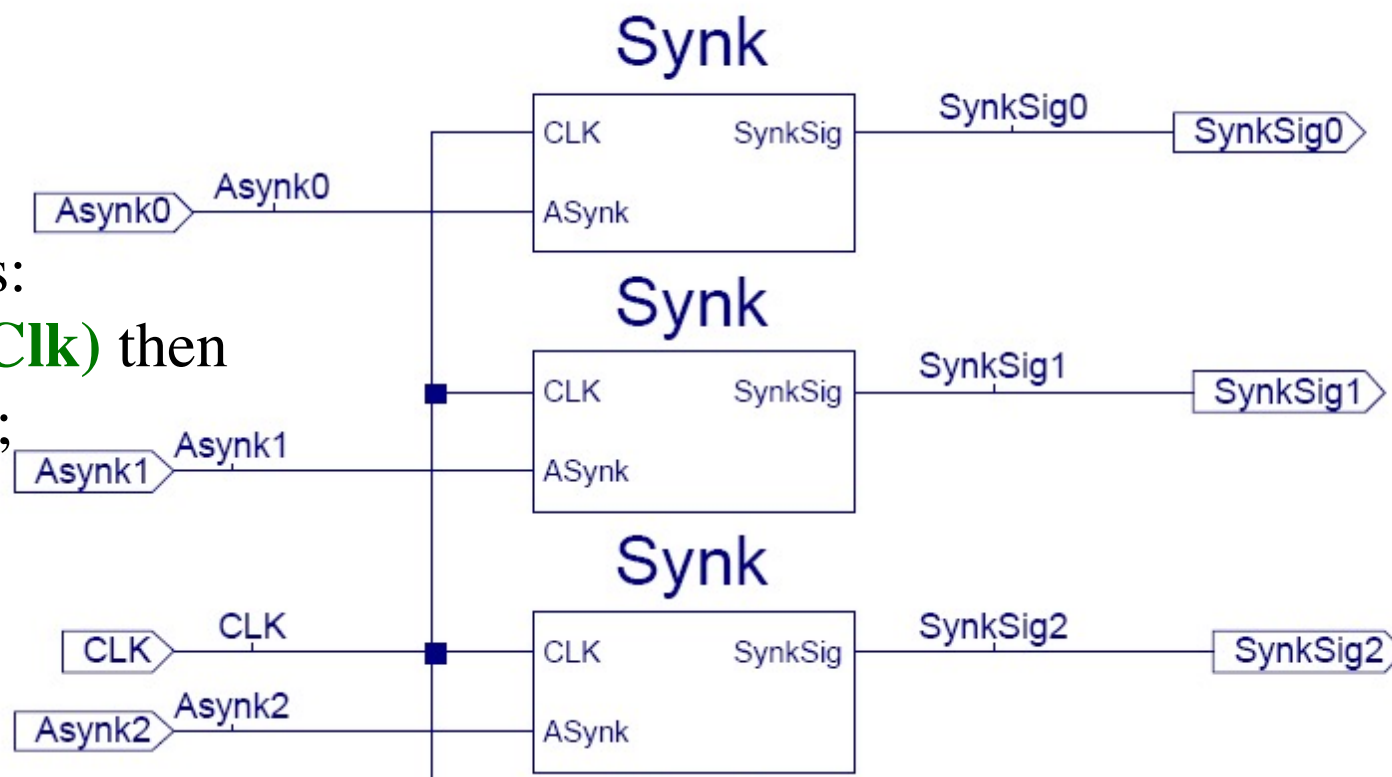VHDL I process:
If **rising_edge(Clk)** then
Hsynk<=Asynk;
Synk<=Hsynk;



Exempel paritetskontroll.

```
[loop_label:] FOR <identifier> IN <range> LOOP  
statements  
END LOOP [loop_label:];
```

```
ARCHITECTURE arch_Par_Check OF Par_Check IS
```

```
BEGIN
```

```
  p0: PROCESS (a) IS
```

```
    VARIABLE even : std_logic;
```

```
  BEGIN
```

```
    even:='0';
```

```
    FOR i IN a'RANGE LOOP
```

```
      IF a(i)='1' THEN
```

```
        even := not even;
```

```
      END IF;
```

```
    END LOOP;
```

```
    y<= even;
```

```
  END process p0;
```

```
END ARCHITECTURE arch_Par_Check;
```

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY Par_Check IS
```

```
  PORT(a:IN STD_LOGIC_vector (7 downto 0);  
        y:OUT STD_LOGIC);
```

```
END Par_Check;
```



Strukturell VHDL.


Components

Exempel


Vi vill bygga en två-bitars adderare.

Vi börjar med att bygga en full adderare.

 Sedan kopplar vi samman två av dessa för att få vår två bitars adderare.



One-bit adder

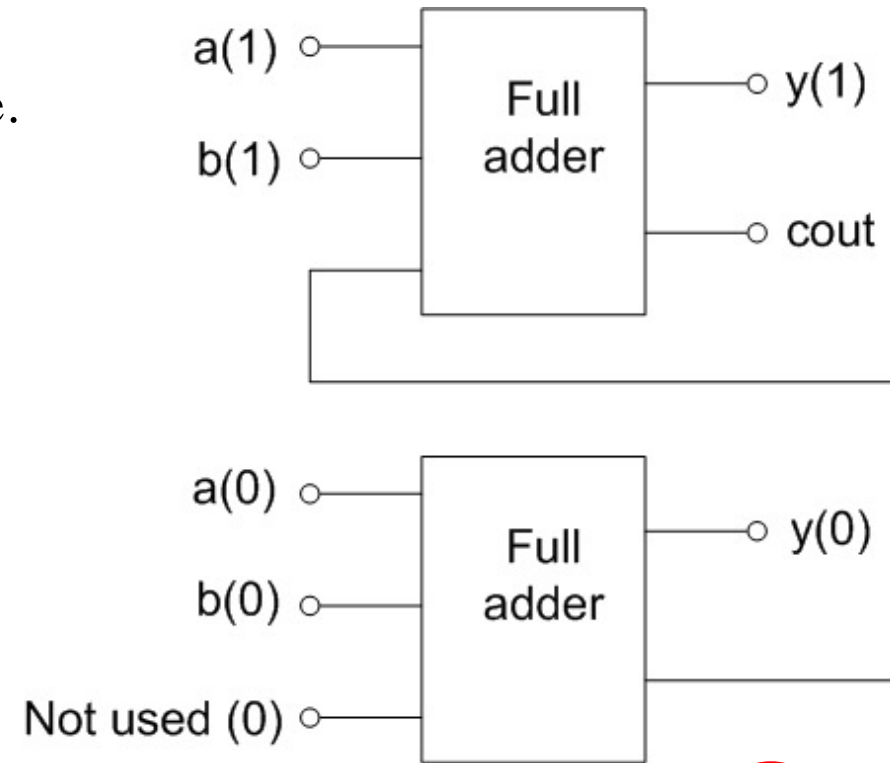


Two-bit adder



```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY full_adder IS
    PORT (
        a:IN  STD_LOGIC;
        b:IN  STD_LOGIC;
        cin:IN STD_LOGIC;
        y:OUT  STD_LOGIC;
        cout:OUT STD_LOGIC);
END full_adder;
```

Våran heladderare

 

```
ARCHITECTURE arch_full_adder OF full_adder IS
BEGIN
    y<=a XOR b XOR cin;
    cout<=(a AND b) OR
        (a AND cin) OR
        (b AND cin);
END arch_full_adder;
```

Separata rader ökar läsbarheten



Vi går vidare till två bits adderaren.

```
-- Vi har entiteten
```

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY adder_2_bit IS
```

```
    PORT (    a:IN STD_LOGIC_VECTOR(1 DOWNTO 0);
```

```
            b:IN STD_LOGIC_VECTOR(1 DOWNTO 0);
```

```
            y:OUT STD_LOGIC_VECTOR(1 DOWNTO 0);
```

```
            cout:OUT STD_LOGIC);
```

```
END adder_2_bit;
```




```

ARCHITECTURE arch_adder_2 OF adder_2 IS
COMPONENT full_adder IS
    PORT (
        a:IN STD_LOGIC;
        b:IN STD_LOGIC;
        cin:IN STD_LOGIC;
        y:OUT STD_LOGIC;
        cout:OUT STD_LOGIC);
END COMPONENT full_adder;
    SIGNAL cint:STD_LOGIC;
BEGIN
    U0:COMPONENT full_adder
        PORT MAP (a=>a(0),b=>b(0),
                  cin=>'0',y=>y(0),cout=>cint);
    U1:COMPONENT full_adder
        PORT MAP (a=>a(1),b=>b(1),
                  cin=>cint,y=>y(1),cout=>cout);
END arch_adder_2;

```

Komponent deklaration

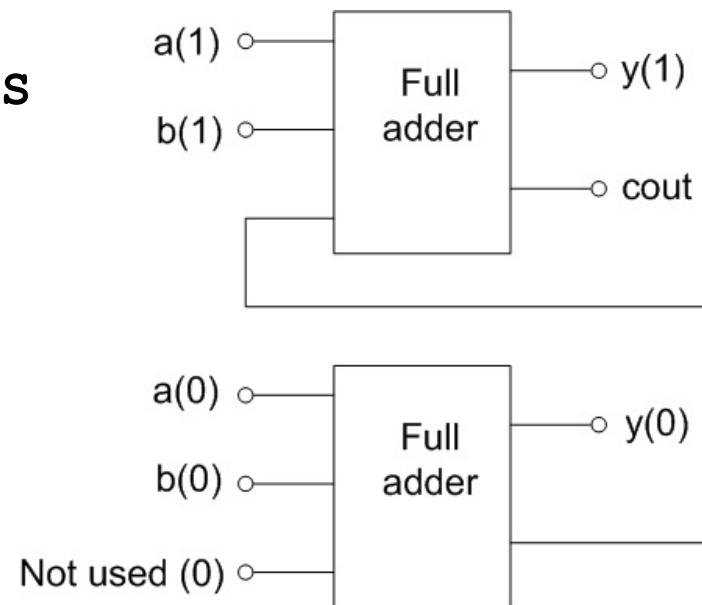

Komponent
instanser





Komponent deklARATIONEN är identisk med 2-bitars fallet
(Eftersom det är samma komponent)

```
COMPONENT full_adder IS  
  PORT (  
    a:IN STD_LOGIC;  
    b:IN STD_LOGIC;  
    cin:IN STD_LOGIC;  
    y:OUT STD_LOGIC  
    cout:OUT STD_LOGIC);  
END COMPONENT full_adder;
```



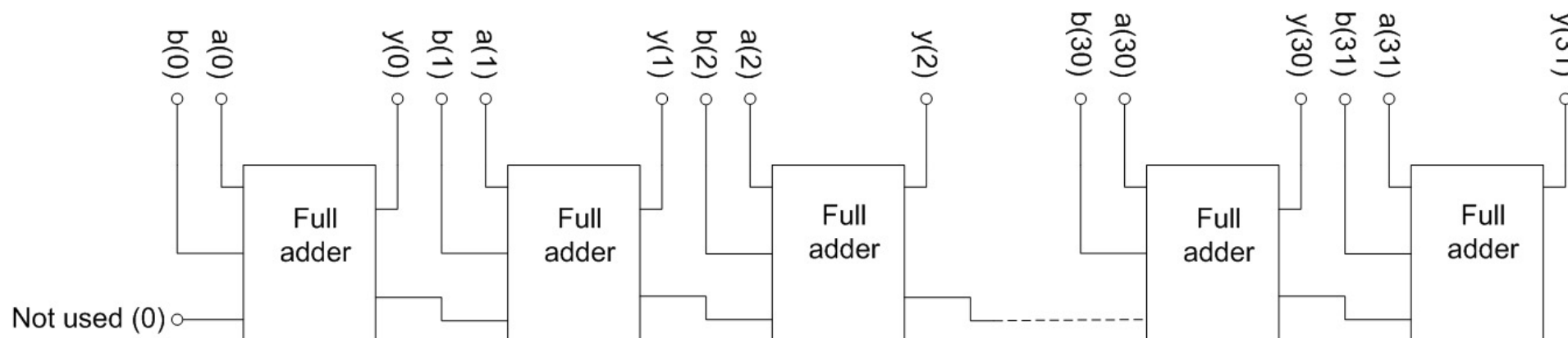Vi måste ändra i arkitekturen där komponenten instantieras.



 

ARCHITECTURE arch_adder_32_bit **OF** adder_32_bit **IS**

{declaration of component full_adder}

SIGNAL cint:STD_LOGIC_VECTOR(30 **DOWNTO** 0);

Signal för
överföring av "carry"

BEGIN

U0:COMPONENT full_adder

PORT MAP (a=>a(0), b=>b(0), cin=>'0',

y=>y(0), cout=>cint(0));

Ingen cin

G:FOR i IN 1 TO 30 **GENERATE**

Ui:COMPONENT full_adder

PORT MAP (a=>a(i), b=>b(i), cin=>cint(i-1),

y=>y(i), cout=>cint(i));

Component
instantiations

END GENERATE;

U31:COMPONENT full_adder

PORT MAP (a=>a(31), b=>b(31), cin=>cint(30),

y=>y(31));


Ripple carry

END arch_adder_32_bit;

MSB och LSB måste instantieras separat!

cout är inte ansluten



 

Låt oss titta närmare på genereringen av bit 1 till 30

Generate statement måste ha en label

Index variabeln behöver inte deklareras

```
G: FOR i IN 1 TO 30 GENERATE
  Ui: COMPONENT full_adder
    PORT MAP (a=>a(i), b=>b(i), cin=>cin(i-1),
               y=>y(i), cout=>cint(i));
  END GENERATE;
```

Vi behöver inte separata namn för de olika komponenterna

Vi kan se här att vi har en loop som kommer att vecklas ut till 30 en bitars adderare.

VHDL FSM - Reduce 1s example

```

entity Reduce1Moor is
  port ( Clk  : in  std_logic;
         I    : in  std_logic;
         Reset : in  std_logic;
         O    : out std_logic);
end Reduce1Moor;

```

```

architecture BEHAVIORAL of Reduce1Moor is
  type state_type is (zero,one1,two1s); --Tillståndsdeklaration
  signal state:state_type;

```

```

begin

```

```

  -----

```

```


  -----

```

```

end BEHAVIORAL;

```

 

Tillståndskodning (på ett ställe, enkelt att ändra)

```


architecture BEHAVIORAL of Reduce1Moor is
  constant zero : std_logic_vector (1 downto 0) := "00";
  constant one1  : std_logic_vector (1 downto 0) := "01";
  constant two1s : std_logic_vector (1 downto 0) := "10";
  signal state : std_logic_vector (1 downto 0);

```

```

ASM_P: process(Clk,Reset) -- Synkron process
begin
  if Reset = '1' then -- Asynkron reset
    state<=zero; -- Reset tillstånd
  elsif Clk'event and Clk='1' then
    state<=next_state
  end if;
end process ASM_P;

```

 

```

-- Kombinatorisk process
next_s:process(state,I)
begin
  next_state <=zero
  case state is
    when zero=> O<='0';
      if I='1' then next_state <=one1;
      end if;
    when one1=> O<='0';
      if I='1' then next_state <=two1s;
      end if;
    when two1s=> O<='1';
      if I='1' then
        next_state <=two1s;
      end if;
    end case;
  end process next_s;

```

```

architecture BEHAVIORAL of Reduce1Mealy is
  type state_type is (zero,one1); --Tillståndsklaration
  signal state:state_type;
  signal next_state:state_type;

```

```

begin
  p1:process(Clk, Reset, next_state)
  begin
    if Clk'event and Clk='1' then
      if Reset = '1' then state<=zero;
        else state<=next_state;
      end if; end if;
    end process p1;

    p2:process(state,I)
    begin
      case state is
        when zero=>
          if I='1' then next_state<=one1; O<='0';
            else next_state<=zero; O<='0';
          end if;
        when one1=>
          if I='1' then next_state<=one1; O<='1';
            else next_state<=zero; O<='0';
          end if;
        when others=> next_state<=zero;
      end case;
    end process p2;
  end BEHAVIORAL;

```

